

RF Amplifier Design

**Alex D. Santiago-Vargas, MSECE
Prof. Dimitrios Peroulis, Ph.D.**

**Purdue University
November 25, 2025**

Outline

- Introduction
- Two-Port Gain Definitions
- Unilateral Case
- Stability
- Biasing and Modes of Operation
- Efficiency
- Case Studies
- Conclusion

Introduction: Where are active circuits used?

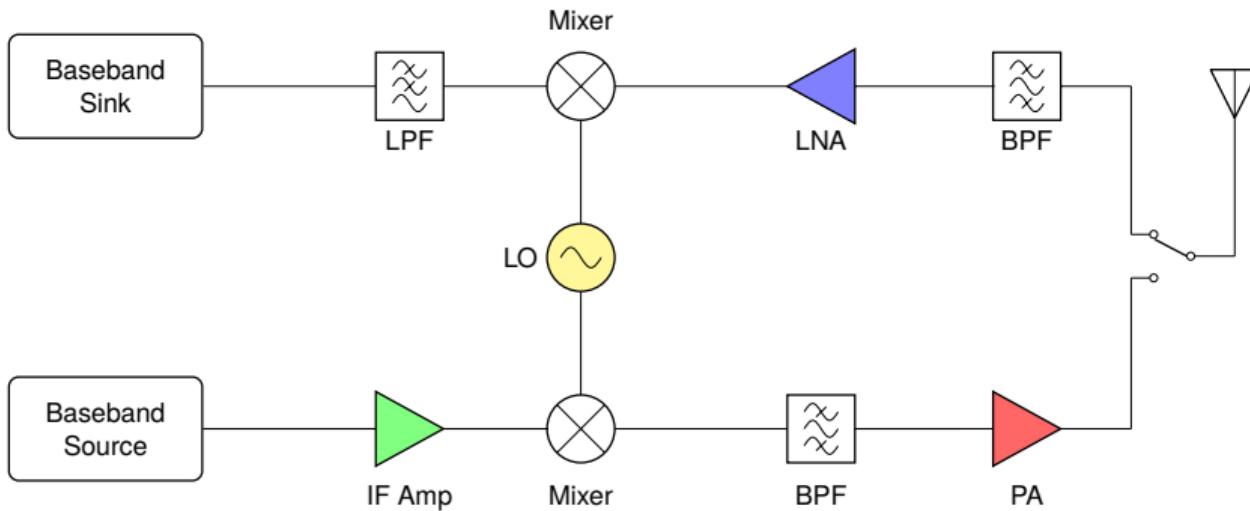


Figure 1: Heterodyne radio highlighting common active components

Introduction: Design Space

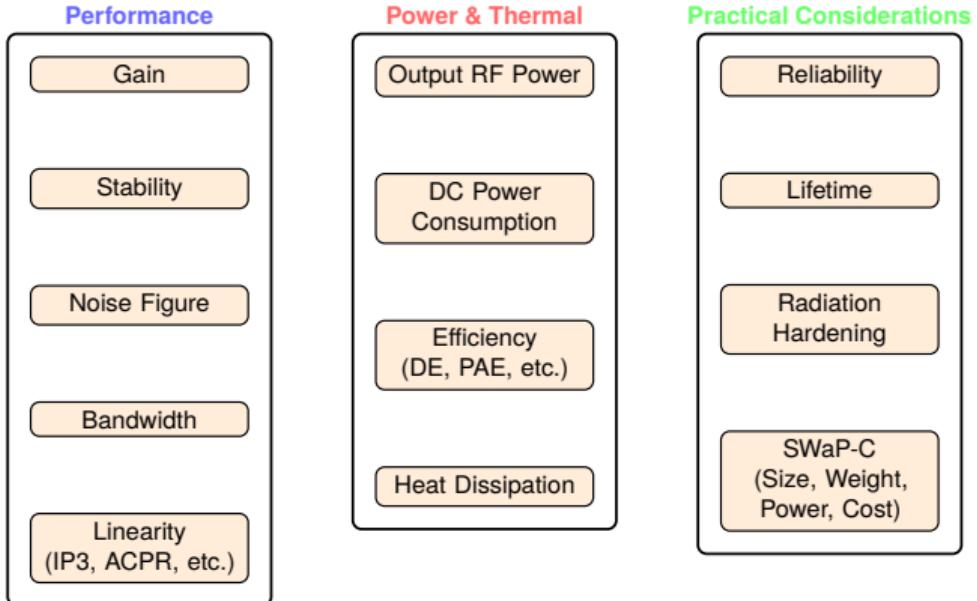


Figure 2: Active Microwave Circuits Design Space

Amplifier circuit excluding DC supply and bias

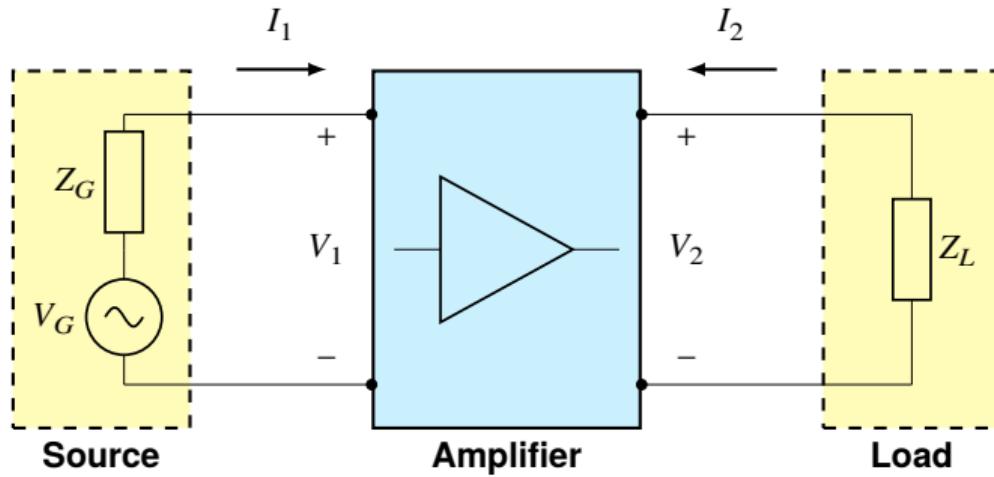


Figure 3: Amplifier circuit excluding DC supply and bias

Generic Amplifier Topology

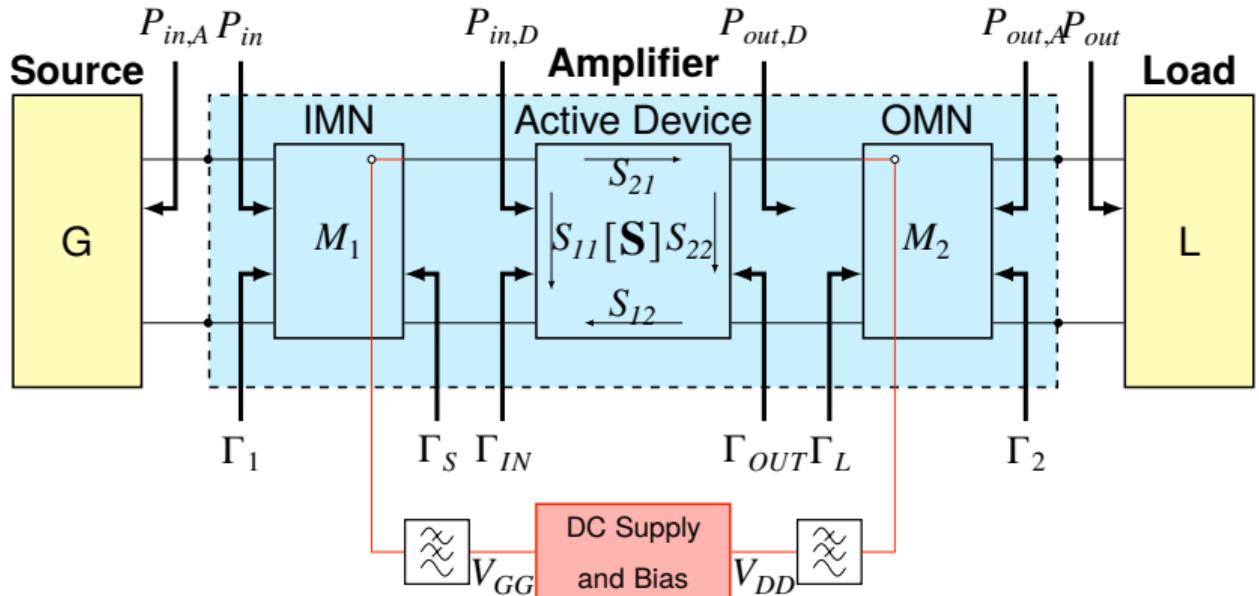


Figure 4: Generic Topology

Power Definitions

Table 1: Power parameters used in gain definitions

Power	Description
$P_{in,A}$	Available input power from the source. $P_{in} \leq P_{in,A}$.
P_{in}	Actual input power delivered to the amplifier.
$P_{in,D}$	Actual input power delivered to the device. $P_{in,D} \leq P_{in}$.
$P_{out,D}$	Available device output power of the device.
$P_{out,A}$	Available amplifier output power. $P_{out,A} \leq P_{out,D}$.
P_{out}	Actual output power delivered to load. Amplifier output power. $P_{out} \leq P_{out,A}$.

Reflection Coefficients for Two-Port Networks

Recall the input and output reflection coefficients Eqs. (1a) and (1b) of a device are calculated from the device S matrix along with the source and load (Γ_S and Γ_L).

$$\Gamma_{IN} = S_{11} + \frac{S_{21}S_{12}\Gamma_L}{1 - S_{22}\Gamma_L} \quad (1a)$$

$$\Gamma_{OUT} = S_{22} + \frac{S_{21}S_{12}\Gamma_S}{1 - S_{11}\Gamma_S} \quad (1b)$$

Power Gain


System: $G = \frac{P_L}{P_{in}} = |S_{21}|^2 \frac{(1 - |\Gamma_L|^2)}{(1 - |\Gamma_{IN}|^2) |1 - S_{22}\Gamma_L|^2}$ (2a)

Transducer: $G_T = \frac{P_L}{P_{in,A}} = |S_{21}|^2 \frac{(1 - |\Gamma_S|^2)(1 - |\Gamma_L|^2)}{|1 - \Gamma_{IN}\Gamma_S|^2 |1 - S_{22}\Gamma_L|^2}$ (2b)

Power: $G_P = \frac{P_L}{P_{in,D}} = |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2 (1 - |\Gamma_{IN}|^2)}$ (2c)

Available: $G_A = \frac{P_{out,A}}{P_{in,A}} = |S_{21}|^2 \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2 (1 - |\Gamma_{OUT}|^2)}$ (2d)

Why is matching needed?

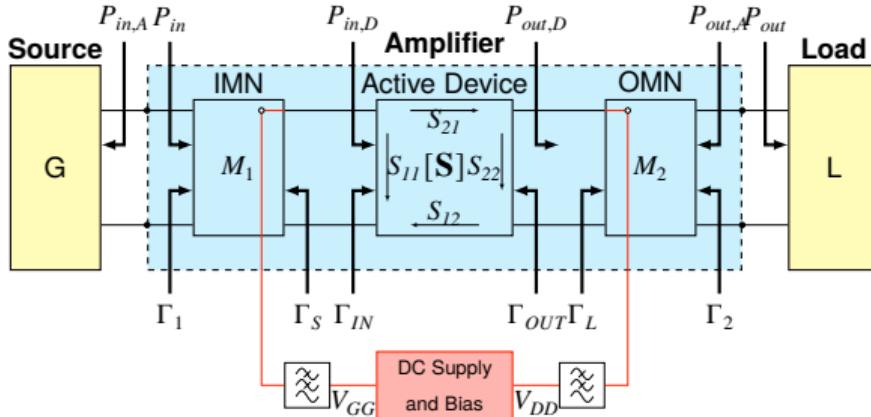

$$G_T = |S_{21}|^2 \frac{(1 - |\Gamma_L|^2)}{(1 - |\Gamma_{IN}|^2) |1 - S_{22}\Gamma_L|^2}$$

$$\Gamma_S = \Gamma_L = 0 \Rightarrow G_T = |S_{21}|^2$$

Mismatch Loss

- The source mismatch factor quantize the portion of the available power that is delivered to the device at the input.

$$M_S = \frac{P_{in,D}}{P_{in,A}} = \frac{(1 - |\Gamma_S|^2)(1 - |\Gamma_{IN}|^2)}{|1 - \Gamma_{IN}\Gamma_S|^2} \quad (3)$$

- The load mismatch factor quantize the portion of the device available output power that is delivered to the load.

$$M_L = \frac{P_L}{P_{out,A}} = \frac{(1 - |\Gamma_L|^2)(1 - |\Gamma_{OUT}|^2)}{|1 - \Gamma_{OUT}\Gamma_L|^2} \quad (4)$$

- If $\Gamma_{IN} = \Gamma_S^* \Rightarrow M_S = 1$. If $\Gamma_{OUT} = \Gamma_L^* \Rightarrow M_L = 1$.

Unifying power gains

Recall: $G_T = \frac{P_L}{P_{in,A}}$, $G_P = \frac{P_L}{P_{in,D}}$, $G_A = \frac{P_{out,A}}{P_{in,A}}$


The transducer gain can be represented in terms of the power and available gain using the source and load mismatch losses.

$$G_T = \frac{P_{in,D}}{P_{in,A}} \frac{P_L}{P_{in,D}} = M_S G_P \quad (5)$$

$$G_T = \frac{P_{out,A}}{P_{in,A}} \frac{P_L}{P_{out,A}} = G_A M_L \quad (6)$$

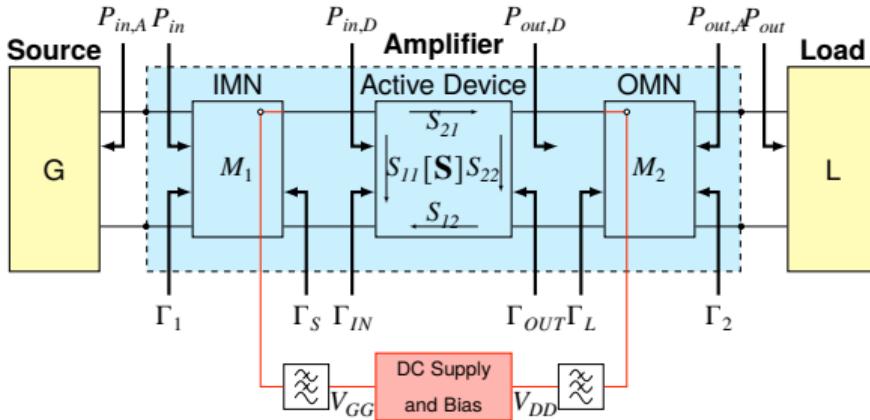Example on Power Gain

Calculate G_T , G_P , G_A , M_S , M_L with the following [1]:



$$\Gamma_S = 0.5\angle 120^\circ, \quad \Gamma_L = 0.4\angle 90^\circ$$

$$S = \begin{bmatrix} 0.6\angle -160^\circ & 0.045\angle 16^\circ \\ 2.5\angle 30^\circ & 0.5\angle -90^\circ \end{bmatrix}$$

Example on Power Gain

$$\begin{aligned}\Gamma_{IN} &= S_{11} + \frac{S_{21}S_{12}\Gamma_L}{1 - S_{22}\Gamma_L} \\&= 0.6\angle - 160^\circ + \frac{(2.5\angle 30^\circ)(0.045\angle 16^\circ)(0.4\angle 90^\circ)}{1 - (0.5\angle - 90^\circ)(0.4\angle 90^\circ)} \\&= 0.627\angle - 164.6^\circ\end{aligned}$$

$$\begin{aligned}\Gamma_{OUT} &= S_{22} + \frac{S_{21}S_{12}\Gamma_S}{1 - S_{11}\Gamma_S} \\&= 0.4\angle 90^\circ + \frac{(2.5\angle 30^\circ)(0.045\angle 16^\circ)(0.5\angle 120^\circ)}{1 - (0.6\angle - 160^\circ)(0.5\angle 120^\circ)} \\&= 0.471\angle - 97.63^\circ\end{aligned}$$

Example on Power Gain

$$G_T = |S_{21}|^2 \frac{(1 - |\Gamma_L|^2)}{(1 - |\Gamma_{IN}|^2) |1 - S_{22}\Gamma_L|^2} = 9.43 = 9.75 \text{ dB}$$

$$G_P = |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2 (1 - |\Gamma_{IN}|^2)} = 13.51 = 11.31 \text{ dB}$$

$$G_A = |S_{21}|^2 \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2 (1 - |\Gamma_{OUT}|^2)} = 9.55 = 9.8 \text{ dB}$$

Example on Power Gain

$$M_S = \frac{(1 - |\Gamma_S|^2)(1 - |\Gamma_{IN}|^2)}{|1 - \Gamma_{IN}\Gamma_S|^2} = 0.6983 = -1.56 \text{ dB}$$

$$M_L = \frac{(1 - |\Gamma_L|^2)(1 - |\Gamma_{OUT}|^2)}{|1 - \Gamma_{OUT}\Gamma_L|^2} = 0.9874 = -0.055 \text{ dB}$$

Comparing the power gains, $G_T = 9.75 \text{ dB}$, $G_P = 11.31 \text{ dB}$, $G_A = 9.8 \text{ dB}$. This shows that the input matching is not optimal but can provide an extra 1.5 dB of gain.



PURDUE
UNIVERSITY

Elmore Family School of Electrical
and Computer Engineering

Example on Power Gain

Given a source with 0.25 W (24 dBm) of available power

The device input power:

$$P_{in,D} = P_{in,A}M_S = 24 \text{ dBm} - 1.56 \text{ dB} = 22.44 \text{ dBm}$$

The power delivered to the load:

$$P_L = G_T P_{in,A} = 9.75 \text{ dB} + 24 \text{ dBm} = 33.75 \text{ dBm}$$

The rest of the powers can be calculated similarly, using the input power, power gains, and mismatch losses.



PURDUE
UNIVERSITY

Elmore Family School of Electrical
and Computer Engineering

Unilateral Transducer Gain

Unilateral device: $S_{12} = 0$.

$$G_{TU} = \left(\frac{1 - |\Gamma_S|^2}{|1 - \Gamma_S S_{11}|^2} \right) |S_{21}|^2 \left(\frac{1 - |\Gamma_L|^2}{|1 - \Gamma_L S_{22}|^2} \right) = G_S G_o G_L \quad (9)$$

Which can be decomposed into:

$$G_S = \frac{1 - |\Gamma_S|^2}{|1 - \Gamma_S S_{11}|^2} \quad (10a)$$

$$G_o = |S_{21}|^2 \quad (10b)$$

$$G_L = \frac{1 - |\Gamma_L|^2}{|1 - \Gamma_L S_{22}|^2} \quad (10c)$$


Maximum Unilateral Transducer Gain

A unilateral device can be simply conjugately matched by $\Gamma_S = S_{11}^*$ and $\Gamma_L = S_{22}^*$. In this case, the max unilateral transducer gain is

$$G_{TU,max} = |S_{21}|^2 \left(\frac{1}{1 - |S_{11}|^2} \right) \left(\frac{1}{1 - |S_{22}|^2} \right) \quad (11)$$

If the approximation is good enough, this can be a great figure of merit to compare devices as it is only dependent on the S parameters.

Conditions for Stability

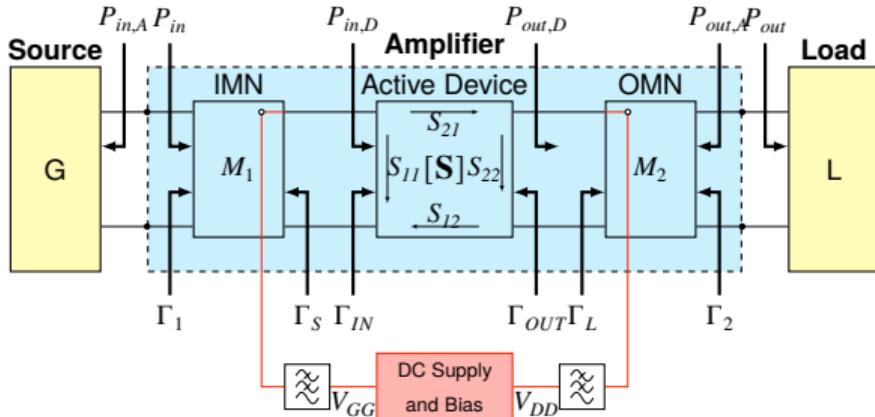

Potentially unstable if:

$$|\Gamma_S \Gamma_{IN}| > 1 \quad (12a)$$

$$|\Gamma_L \Gamma_{OUT}| > 1 \quad (12b)$$

Conditions for Stability

Assumption: $|\Gamma_S| \leq 1$ and $|\Gamma_L| \leq 1$

In this case, stability can be ensured if

$$|\Gamma_S \Gamma_{IN}| = \left| \Gamma_S S_{11} + \frac{S_{21} S_{12} \Gamma_S \Gamma_L}{1 - S_{22} \Gamma_L} \right| < 1 \quad (13a)$$

$$|\Gamma_L \Gamma_{OUT}| = \left| \Gamma_L S_{22} + \frac{S_{21} S_{12} \Gamma_S \Gamma_L}{1 - S_{11} \Gamma_S} \right| < 1 \quad (13b)$$

for all $|\Gamma_S| \leq 1$ and $|\Gamma_L| \leq 1$.

The equations can be solved for Γ_S and Γ_L taking the form of the equation for a circle $|\Gamma - c| = |r|$.

Input Stability Circles

$$\left| \Gamma_S - \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} \right| = \left| \frac{S_{12}S_{21}}{|S_{11}|^2 - |\Delta|^2} \right| \quad (14)$$

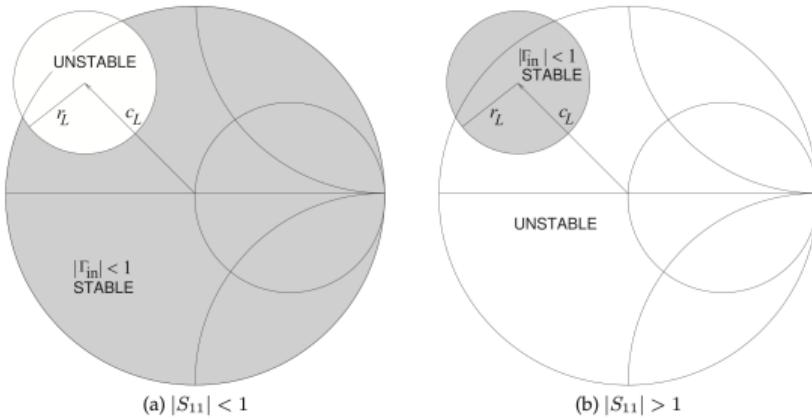


Figure 5: Input Stability Circles

Output Stability Circles

$$\left| \Gamma_L - \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \right| = \left| \frac{S_{12}S_{21}}{|S_{22}|^2 - |\Delta|^2} \right| \quad (15)$$

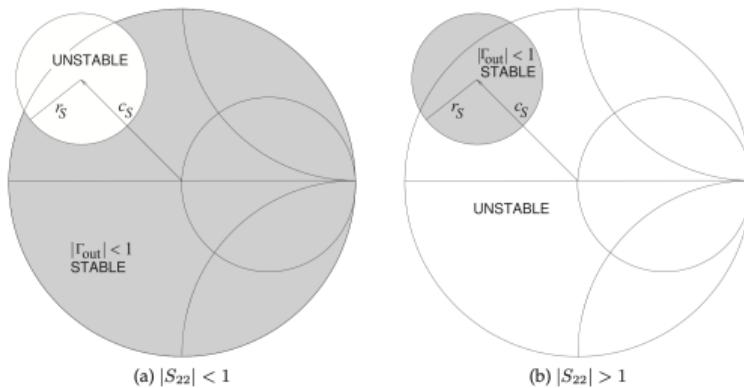


Figure 6: Output Stability Circles

Rollet's Stability Factor

$$k = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}||S_{21}|} > 1. \quad (16)$$

$$|\Delta| = |S_{11}S_{22} - S_{21}S_{12}| < 1 \quad (17)$$

Note this criteria is only valid within the assumption of $\Gamma_{IN} \leq 1$ and $\Gamma_{OUT} \leq 1$.

Edwards-Sinsky Stability Factor


μ and μ' measure the input and output stability, respectively.

$$\mu = \frac{1 - |S_{11}|^2}{|S_{22} - S_{11}^* \Delta| + |S_{12}S_{21}|} > 1 \quad (18a)$$

$$\mu' = \frac{1 - |S_{22}|^2}{|S_{11} - S_{22}^* \Delta| + |S_{12}S_{21}|} > 1 \quad (18b)$$

Note this criteria is only valid within the assumption of $\Gamma_{IN} \leq 1$ and $\Gamma_{OUT} \leq 1$.

Example on Stability

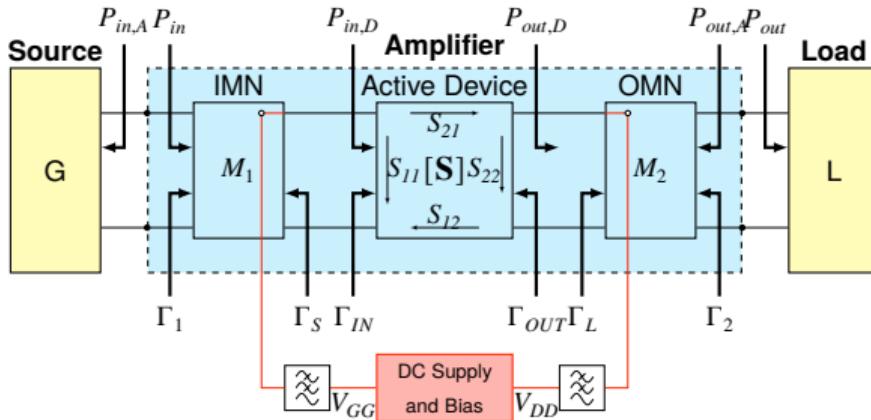

$$S = \begin{bmatrix} 0.65\angle - 95^\circ & 0.035\angle 40^\circ \\ 5\angle 115^\circ & 0.8\angle - 35^\circ \end{bmatrix}$$

Example on Stability


$$k = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}||S_{21}|} = 0.547$$

$$|\Delta| = |S_{11}S_{22} - S_{21}S_{12}| = 0.504$$



$$c_S = 1.79\angle 122^\circ, \quad r_S = 1.04$$

$$c_L = 1.3\angle 48^\circ, \quad r_L = 0.45$$

Example on Stability

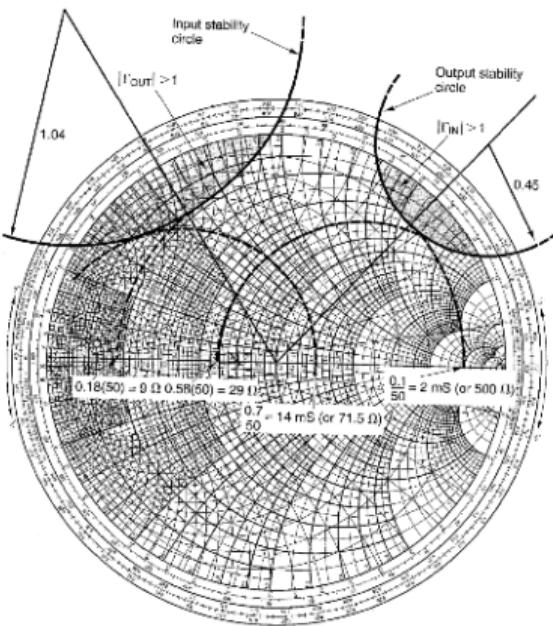


(a) Stability circles

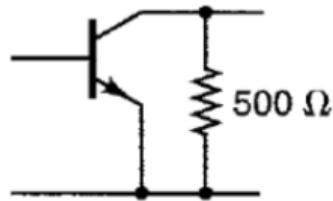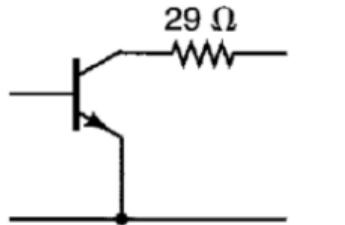


(b) Stabilization circuits

Transistor Biasing

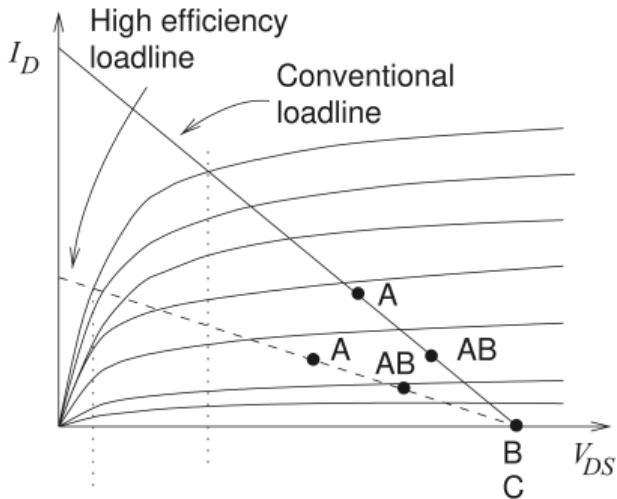

(a) Output transfer

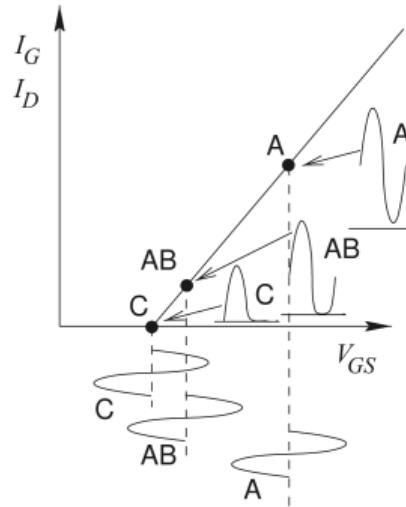

(b) Input transfer

Figure 8: Current-Voltage (I-V) characteristics of a transistor.

Conduction Mode Classes of Operation

Class	Description	Conduction Angle
A	Full cycle conduction	$\theta = 360^\circ$
AB	More than half-cycle conduction	$180^\circ < \theta < 360^\circ$
B	Half cycle conduction	$\theta = 180^\circ$
C	Less than half cycle conduction	$\theta < 180^\circ$

Table 2: Conduction mode classes of operation

Efficiency

$$\eta_D = \frac{P_{RF,out}}{P_{DC}} \quad (19)$$

$$\eta_{PAE} = \frac{P_{RF,out} - P_{RF,in}}{P_{DC}} \quad (20)$$

Table 3: Efficiency in relation to gain for ideal (Class-A) linear amplifier.

Gain (dB)	η_D	η_{PAE}	η_{total}
3	40%	25%	50%
6	44%	37%	50%
10	48%	45%	50%
15	49%	48%	50%
20	50%	50%	50%

Power Amplifier Examples



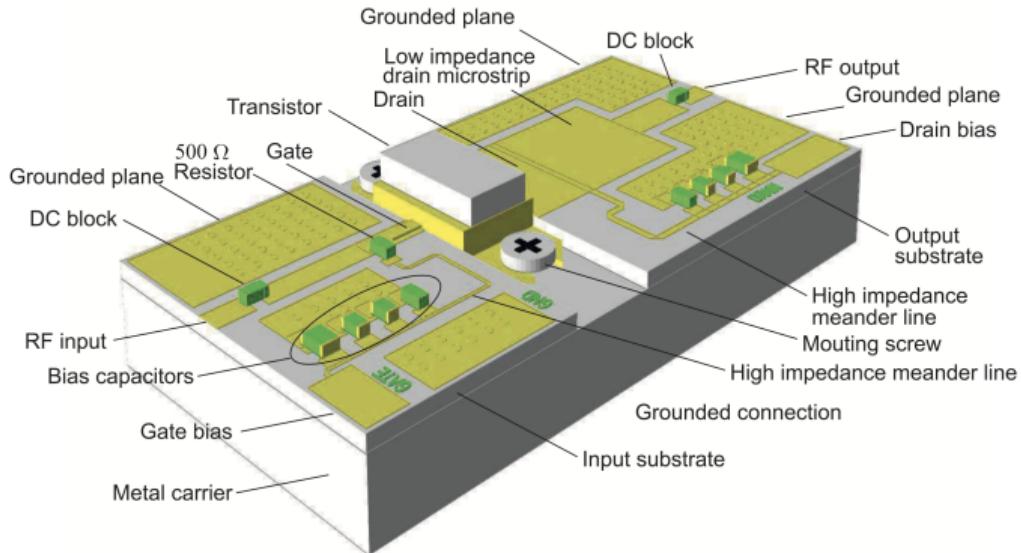


Figure 9: WiMax power amplifier for 3.4 GHz to 3.8 GHz. Taken from [2].

Power Amplifier Examples

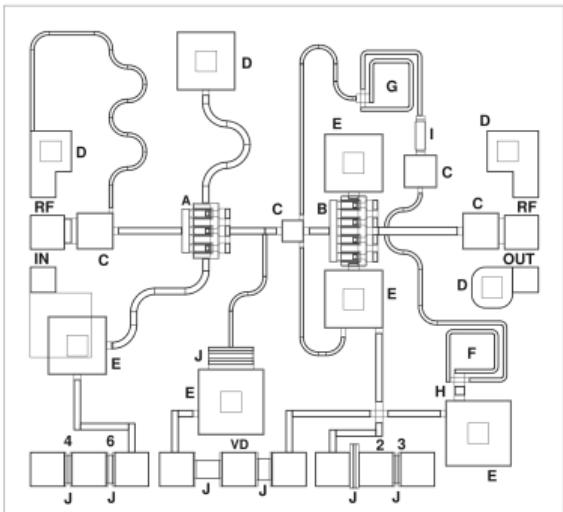

(a) Layout

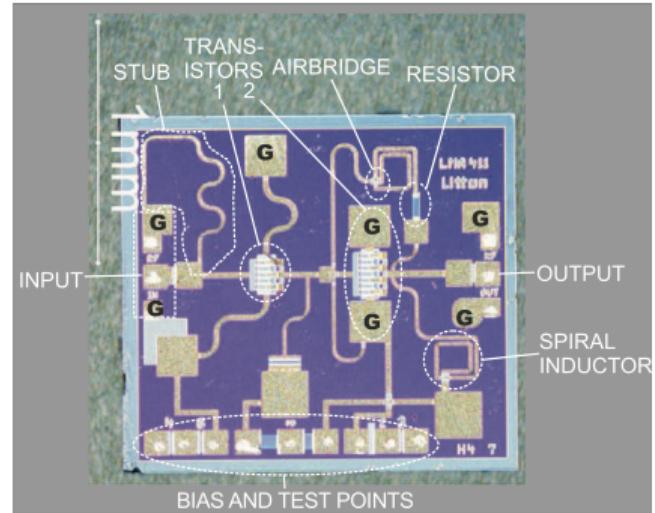

(b) Micrograph

Figure 10: X-Band (8 - 12 GHz) MMIC power amplifier. Taken from [2].



PURDUE
UNIVERSITY

Elmore Family School of Electrical
and Computer Engineering

Power Amplifier Examples

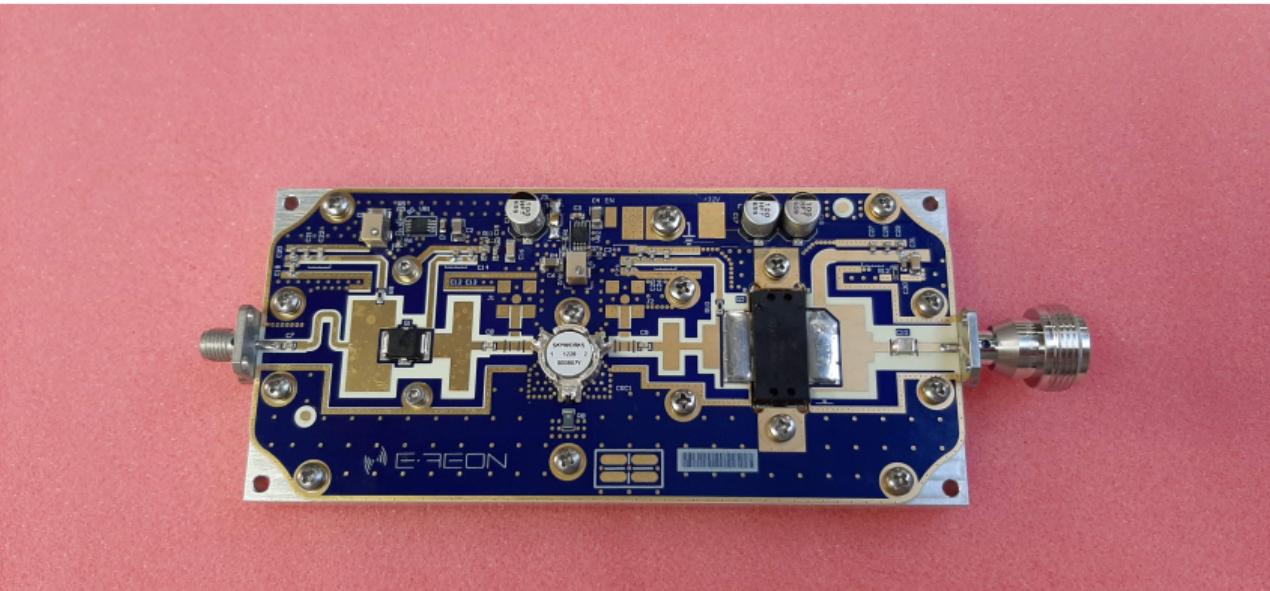


Figure 11: E-REON PowerBlast 300: 2.45 GHz ISM 250 W LDMOS amplifier with 33 dB gain and 60% efficiency [3].

Power Amplifier Examples

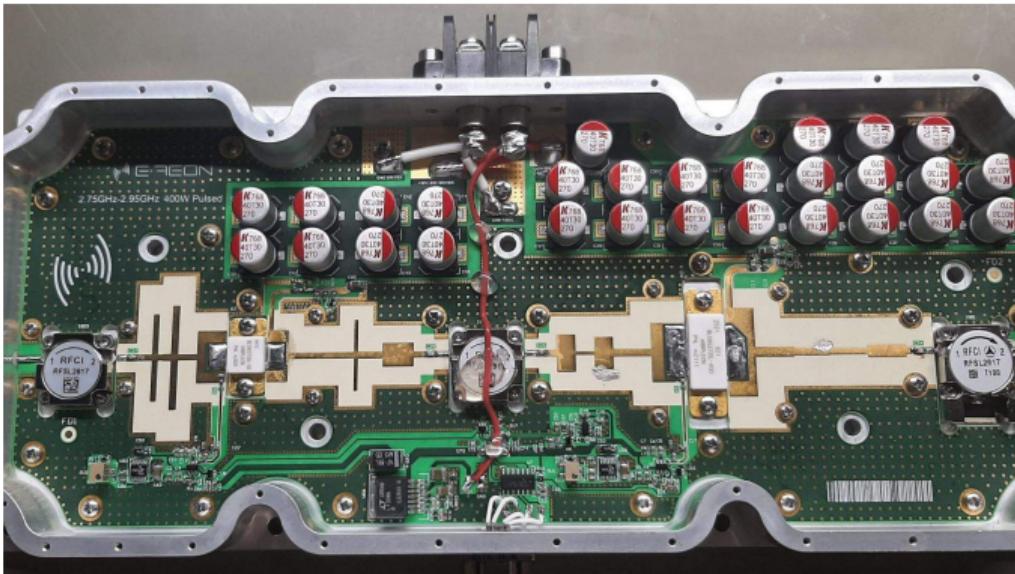


Figure 12: E-REON 2.856 GHz 400 W solid state power amplifier unit used as to drive a Klystron tube in a medical MRI [3].

References I

- [1] G. Gonzalez, *Microwave transistor amplifiers: analysis and design.* Prentice hall New Jersey, 1997, vol. 2.
- [2] M. Steer, *Microwave and RF Design.* NC State University: Raleigh, NC, USA, 2019.
- [3] e-Reon.com, “e-reon — connecting engineers worldwide,” <https://www.e-reon.com>, 2025.

Thank you!